

Student

苏慧哲

Total Points

110 / 100 pts

Question 1**(no title)**

30 / 30 pts

 - 0 pts Correct**- 3 pts** Input 1mV peak voltage means 2mV peak-to-peak voltage, so the gain in your result should be halved.**- 5 pts** Ambiguous explanation**- 5 pts** $Gain = (V_{out,max} - V_{out,min}) / (V_{in,max} - V_{in,min})$ **- 5 pts** Gain<1?**- 30 pts** No submission**- 5 pts** DC input voltage is too far from its correct value, which can cause small voltage gain.**- 20 pts** Incorrect or missing answers**Question 2****(no title)**

40 / 30 pts

 - 0 pts Correct + 10 pts bonus**- 10 pts** (2) partly wrong**- 15 pts** (1) wrong**- 15 pts** (2) wrong**- 2 pts** lack units**- 2 pts** unit wrong**- 5 pts** Click here to replace this description.

Question 3

(no title)

40 / 40 pts

- 0 pts Correct

- 5 pts no detail procedures.

- 5 pts wrong or no simulation

- 40 pts wrong or no answer

Question assigned to the following page: [1](#)

Problem Set #4, EE part


Issue date: Nov. 28, 2020; Deadline: 23:59, Dec. 6, 2020

Student Name: _____ 苏慧哲 _____ Student No.: _____ 2020533009 _____

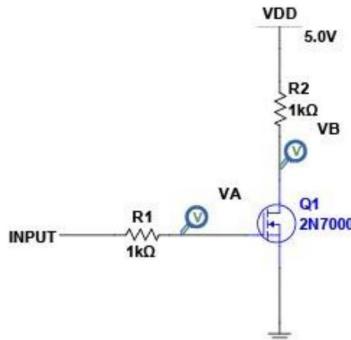
1. Transistor circuit

A MOSFET amplification circuit is given below. The datasheet of NMOS 2N7000 can be found here:

<https://www.onsemi.com/pub/Collateral/2N7000-D.PDF>



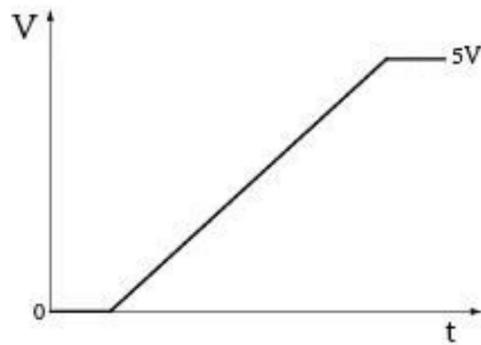- If the input voltage rises from 0 to 5V very slowly, please guess and sketch the waveform of V_A and V_B , and explain the reason (For example, why does the output voltage change when the input voltage reaches a certain value). (10')



V_A and R_1 can be viewed as an open circuit, so the voltage is the same as input voltage.


If input voltage is below threshold voltage, then n-mos is off. In this case, V_B can be considered as being open-circuited, so the voltage of V_B is 5V.

If input voltage is above threshold voltage, then n-mos is on. In this case, the resistance value is much bigger than the resistance value of the n-mos, so the voltage at V_B is very close to 0.


We can learn from the data sheet (Page 3 Figure 2) that the threshold voltage is between 2V and 3V (especially, it's about 2.5V at room temperature).

Therefore, the value of V_B should be 5V at beginning, and drop to a very small value when input voltage reaches threshold voltage, which is around 2.5V. The curve may seem like followed chart:

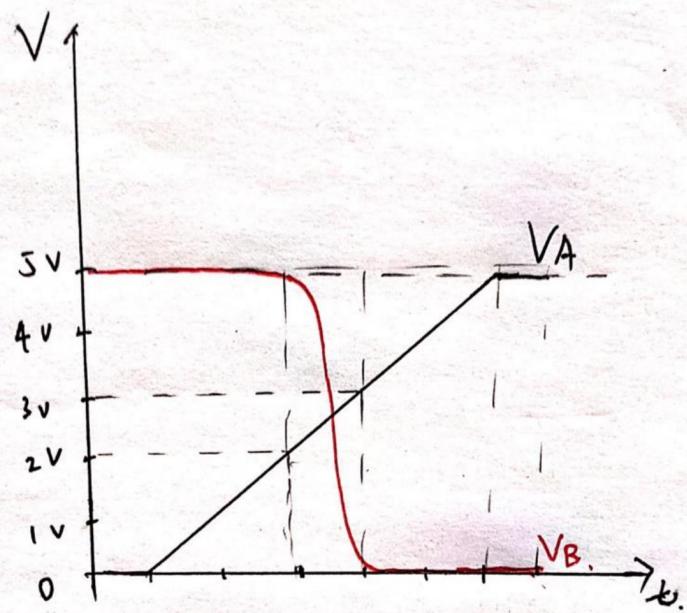
Question assigned to the following page: [1](#)



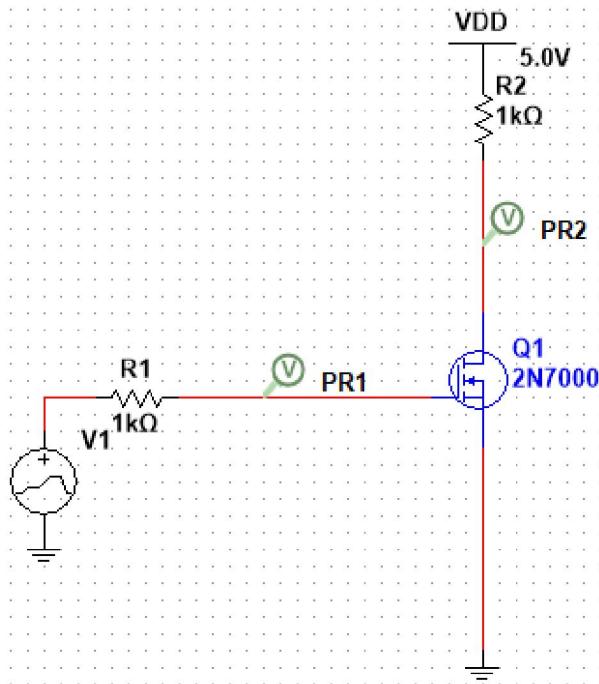
- Build the circuit in Multisim, use ‘DC sweep’ or ‘transient’ simulation to validate your guess. (10’)



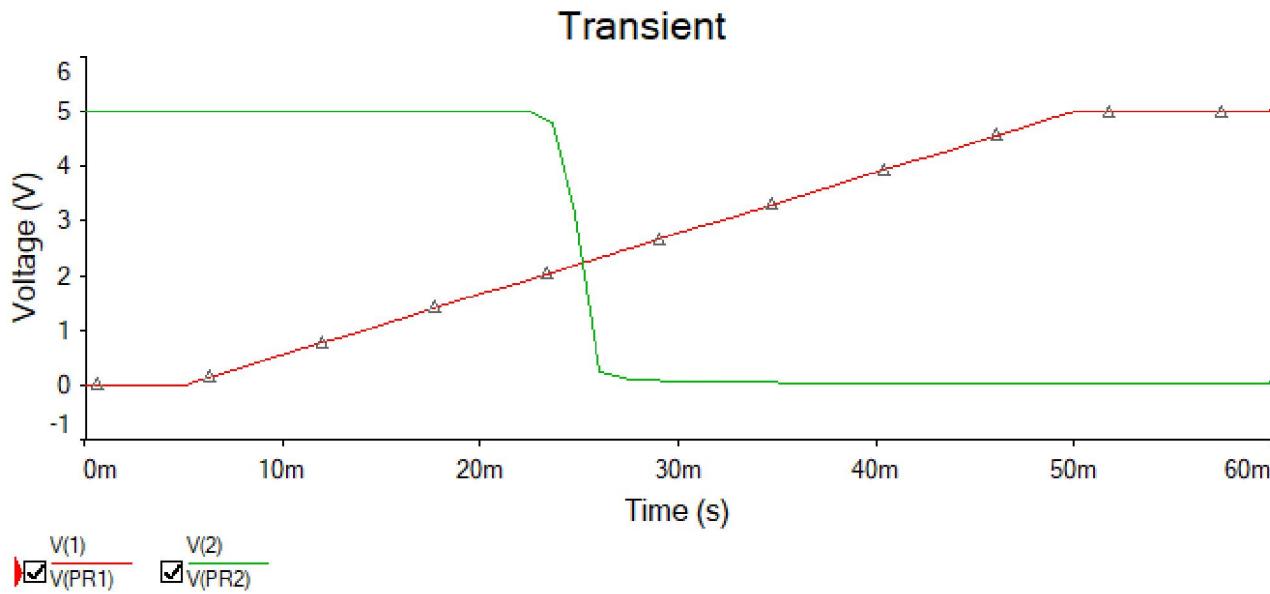
Question assigned to the following page: [1](#)



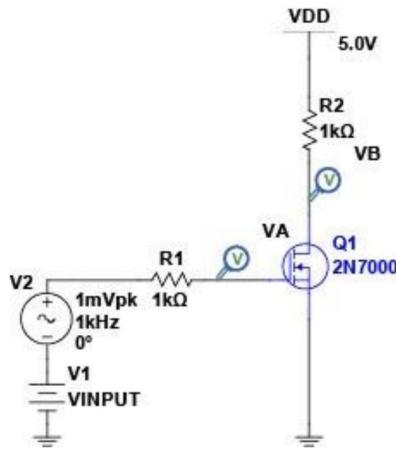
- Find the input value, when $V_B \approx 2.5V$ based on your result in the last question. Then apply an AC voltage (1mV peak voltage) on the DC input. Find the output waveform of V_B , and calculate the voltage gain (neglecting the DC offset, only consider the AC) of this circuit based on your simulation data. (10')



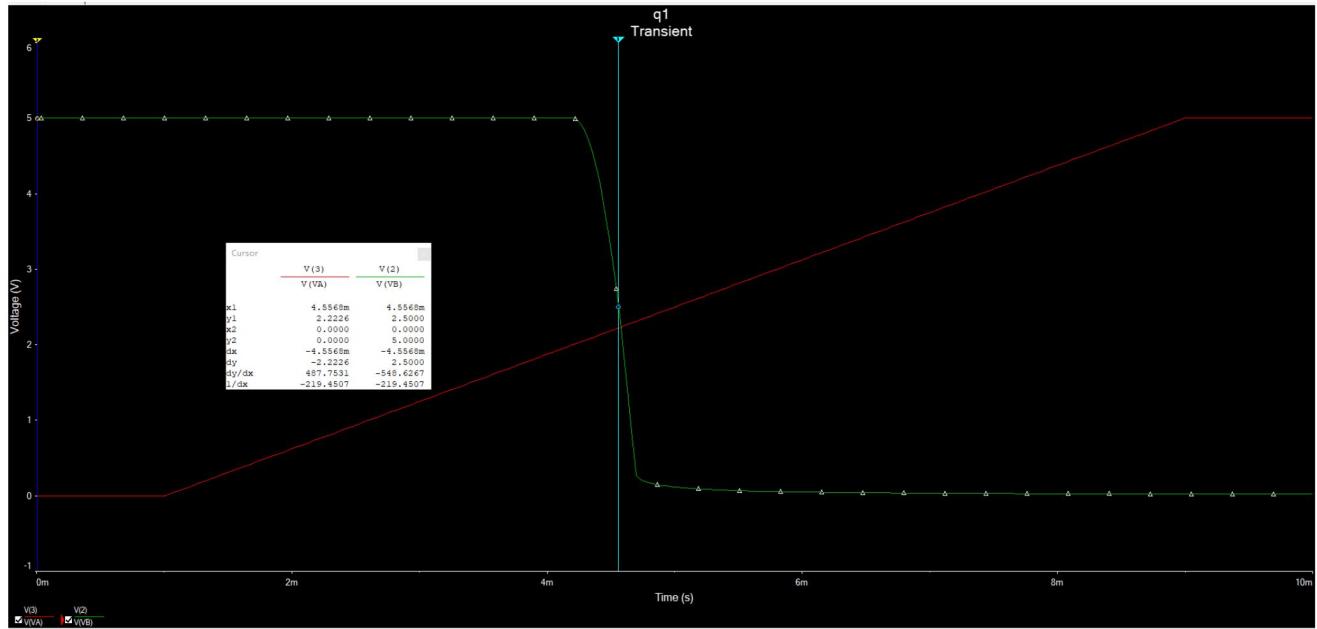
Question assigned to the following page: [1](#)



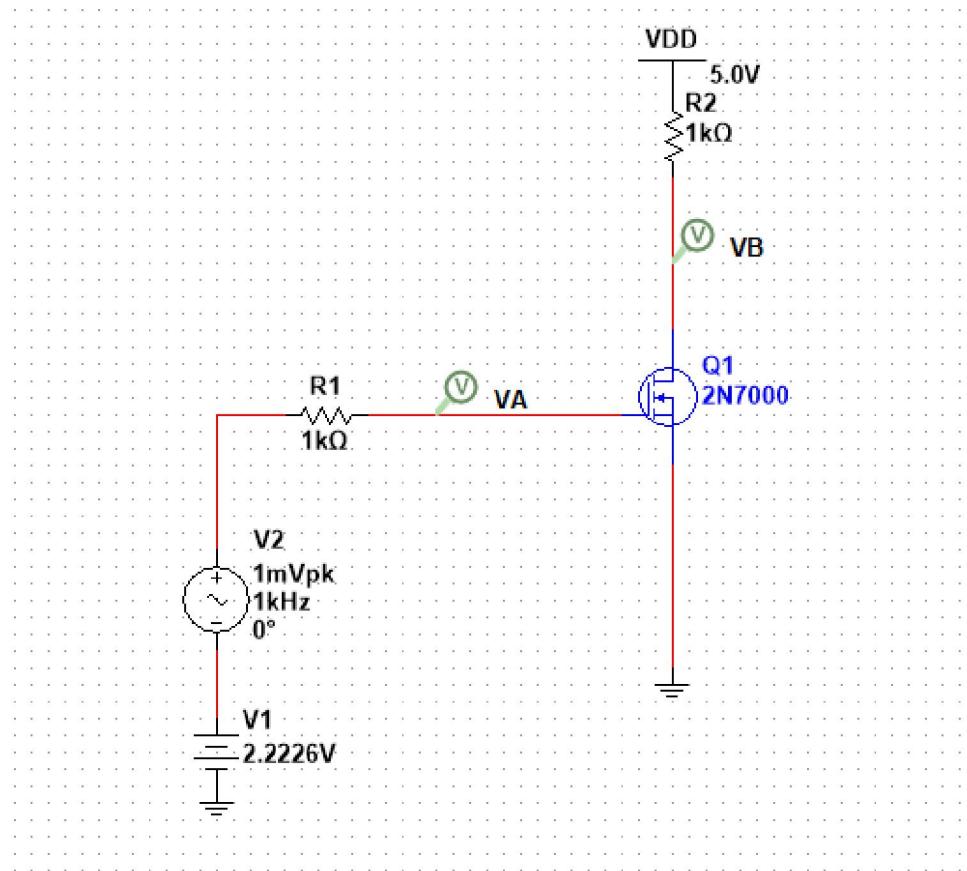We can learn from the chart that VA is 2.2226V when VB is 2.5V.



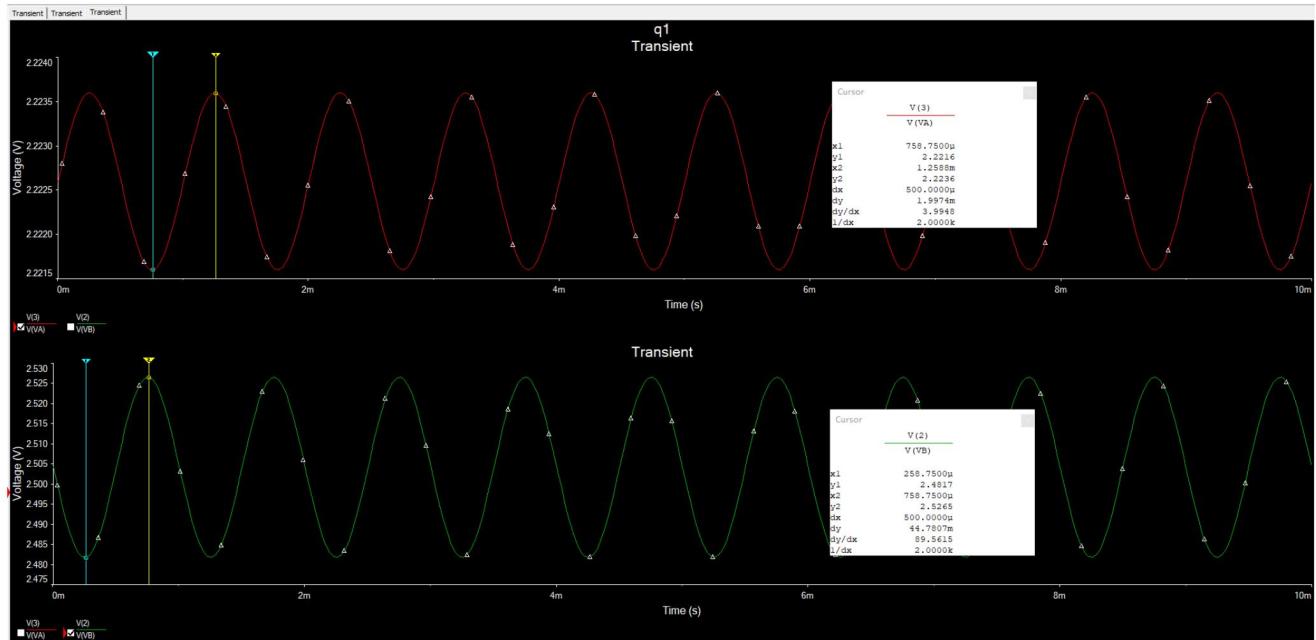Questions assigned to the following page: [2](#) and [1](#)



We can see from the chart. The dy of VA (input voltage) is 1.9974 mV. The dy of VB (output voltage) is 44.7807 mV.


The dy is twice the corresponding amplitude.

The voltage gain is $(dy \text{ of } VB)/(dy \text{ of } VA)$, which is 22.4195.


2. Operational amplifier

Virtual ground is an important method to analyze the circuits with operational amplifiers. (link: <https://baike.baidu.com/item/虚短>). Based on the method of virtual ground, please analyze the output voltage of following circuits. Simulation is not needed in this question, but the procedure of your calculation is necessary.

- Circuit #1 (15')

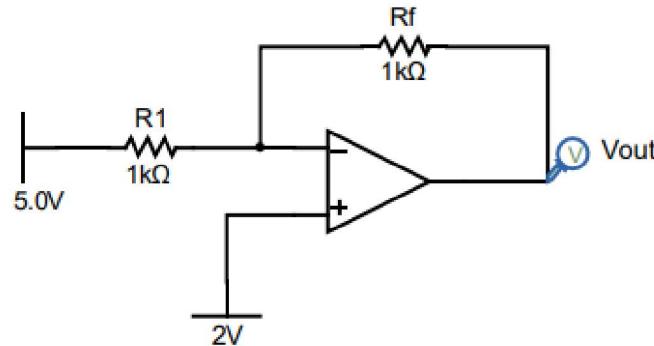

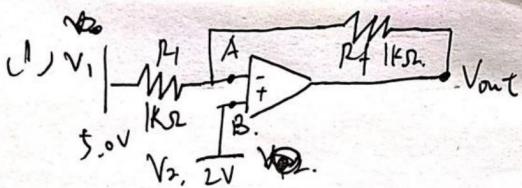Question assigned to the following page: [2](#)



上图 ~~由于~~ 因运算放大器固有的大阻值特性，可以看作“虚地”，~~所以~~ $V_A \approx 0$

$$\text{指从处引出成断路，因此 } I_1 = I_f = \frac{V_1 - V_{out}}{R_1 + R_f} \quad (1)$$

因为上图是负反馈电路，因此可以用“虚短”的概念，即 $V_A = V_B$.

由欧姆定律得：


$$I_1 = \frac{V_1 - V_A}{R_1} = \frac{3V}{1k\Omega} = 3 \times 10^{-3} A.$$

代入(1)式。


$$\begin{aligned} V_{out} &= V_1 - I_1 (R_1 + R_f) \\ &= 5V - 3 \times 10^{-3} \times 2 \times 10^3 V \\ &= -1V \end{aligned}$$

The answer is -1V.

- Circuit #2 (15')

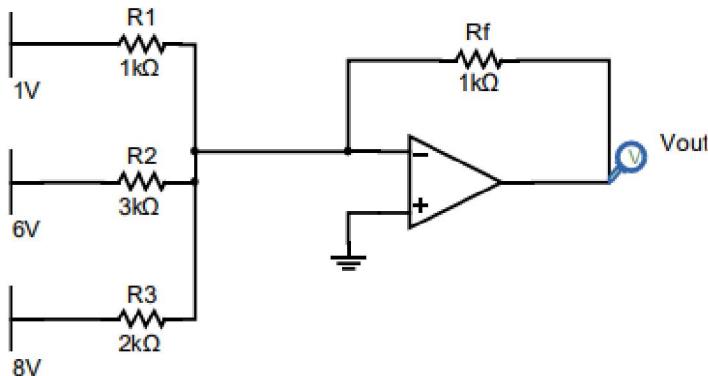

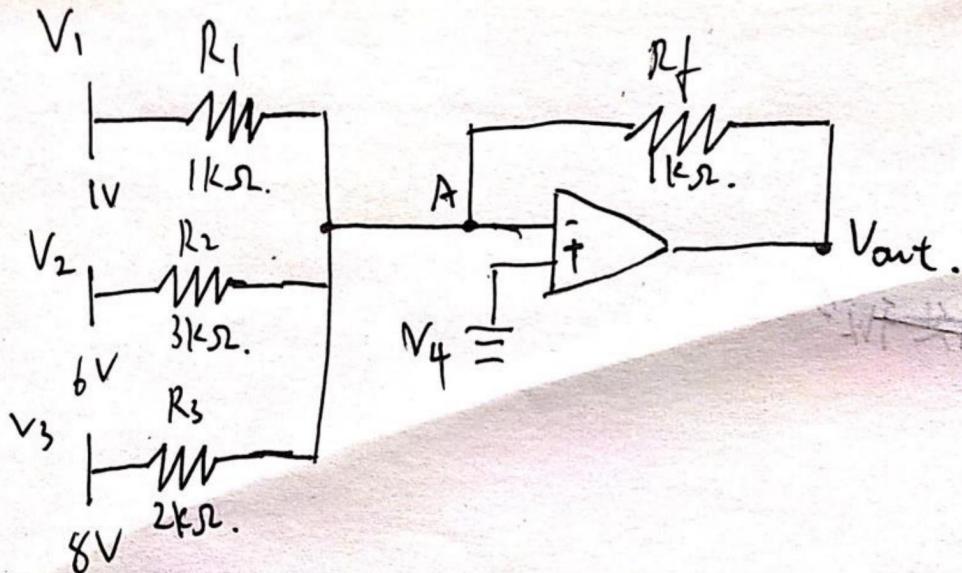Question assigned to the following page: [2](#)



同上一题，这是一个负反馈电路。

首先由“虚短”特性得出

$$I_f = I_1 + I_2 + I_3 \quad \Rightarrow \quad \frac{V_A - V_{out}}{R_f} = \frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3}$$

~~V_A~~ 由“虚短”特性可知 $V_A = V_4$ (虚地接), 所以 $V_A = 0$.

上式可化为.

$$\frac{-V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$\frac{-V_{out}}{1k\Omega} = \frac{1}{10^3}A + \frac{6}{3 \times 10^3}A + \frac{8}{2 \times 10^3}A$$

$$\begin{aligned} V_{out} &= -[1 \times 10^{-3} + 6 \times 10^{-3} + 4 \times 10^{-3}]A \\ &= -7V. \end{aligned}$$

The answer is -7V.

Proof of virtual short.

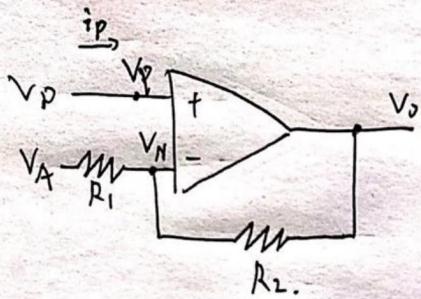Questions assigned to the following page: [2](#) and [3](#)



\because 理想运放放大器输出阻抗无穷大，
即为0，电路“虚短”。

由欧姆定律得：

$$I_N = \frac{V_A - V_N}{R_1} \quad \text{①}$$

$$\therefore V_O = A(V_P - V_N) \quad \text{②}$$

$$\text{由②得: } V_O = V_N - I_N R_2, \text{代入①得:}$$

$$V_N - I_N R_2 = A V_P - A V_N$$

$$V_P = \frac{(1+A)V_N - I_N R_2}{A} \quad \text{③}$$

\because 理想运放放大器 A 为无穷。

$$V_P = \lim_{A \rightarrow \infty} \left(\frac{(1+A)V_N}{A} - \frac{I_N R_2}{A} \right) = \lim_{A \rightarrow \infty} \left(\frac{1}{A} + 1 \right) V_N - \lim_{A \rightarrow \infty} \frac{I_N R_2}{A}. \quad (I_N R_2 \text{ 为有限量})$$

$$V_P = V_N$$

\oplus ~~虚地~~ \therefore 虚短。□.

3. Analog-to-digital converter (ADC)

- Build a 2-bit flash analog-to-digital converter (ADC) in Multisim, the function should confirm to the rule in the following table. Please write down your procedures of design, including your design thought, the simplifications of digital circuit, and the final simulation. (40')

Input voltage	digital output
$0 < V_{in} < 1$	11
$1 < V_{in} < 2$	10
$2 < V_{in} < 3$	01
$3 < V_{in} < 4$	00

Question assigned to the following page: [3](#)

Hints: 1. The ADC example can be found in the slides of lecture #6. 2. Ideal comparator can be found in Analog/ANALOG_VIRTUAL/COMPARATOR_IDEAL




$C_1 =$

- When $V_{in} < 4$, C_4 output 1, otherwise 0
- $V_{in} < 3$, C_3 output 1, otherwise 0
- $V_{in} < 2$, C_2 output 1, otherwise 0
- $V_{in} < 1$, C_1 output 1, otherwise 0

$0 \leq V_{in} < 1$	$out_1 = 1$	$out_0 = 1$
$1 \leq V_{in} < 2$	$out_1 = 1$	$out_0 = 0$
$2 \leq V_{in} < 3$	$out_1 = 0$	$out_0 = 1$
$3 \leq V_{in} \leq 4$	$out_1 = 0$	$out_0 = 0$

	C_4	C_3	C_2	C_1	out_1	out_0
$0 \sim 1$	1	1	1	1	1	1
$1 \sim 2$	1	1	1	0	1	0
$2 \sim 3$	1	1	0	0	0	1
$3 \sim 4$	1	0	0	0	0	0


18

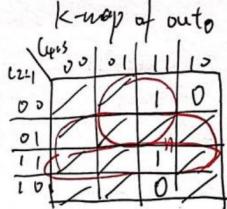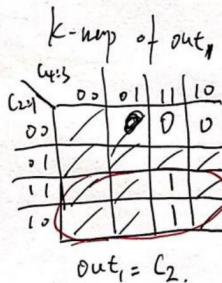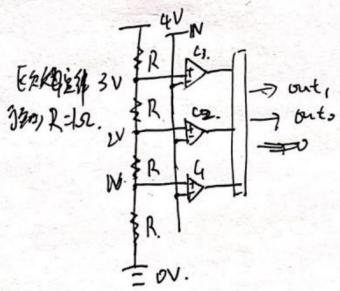

$$out_0 = \overline{C_2} C_3 + \overline{C_4} C_3$$

We can find the C_4 doesn't affect the result.

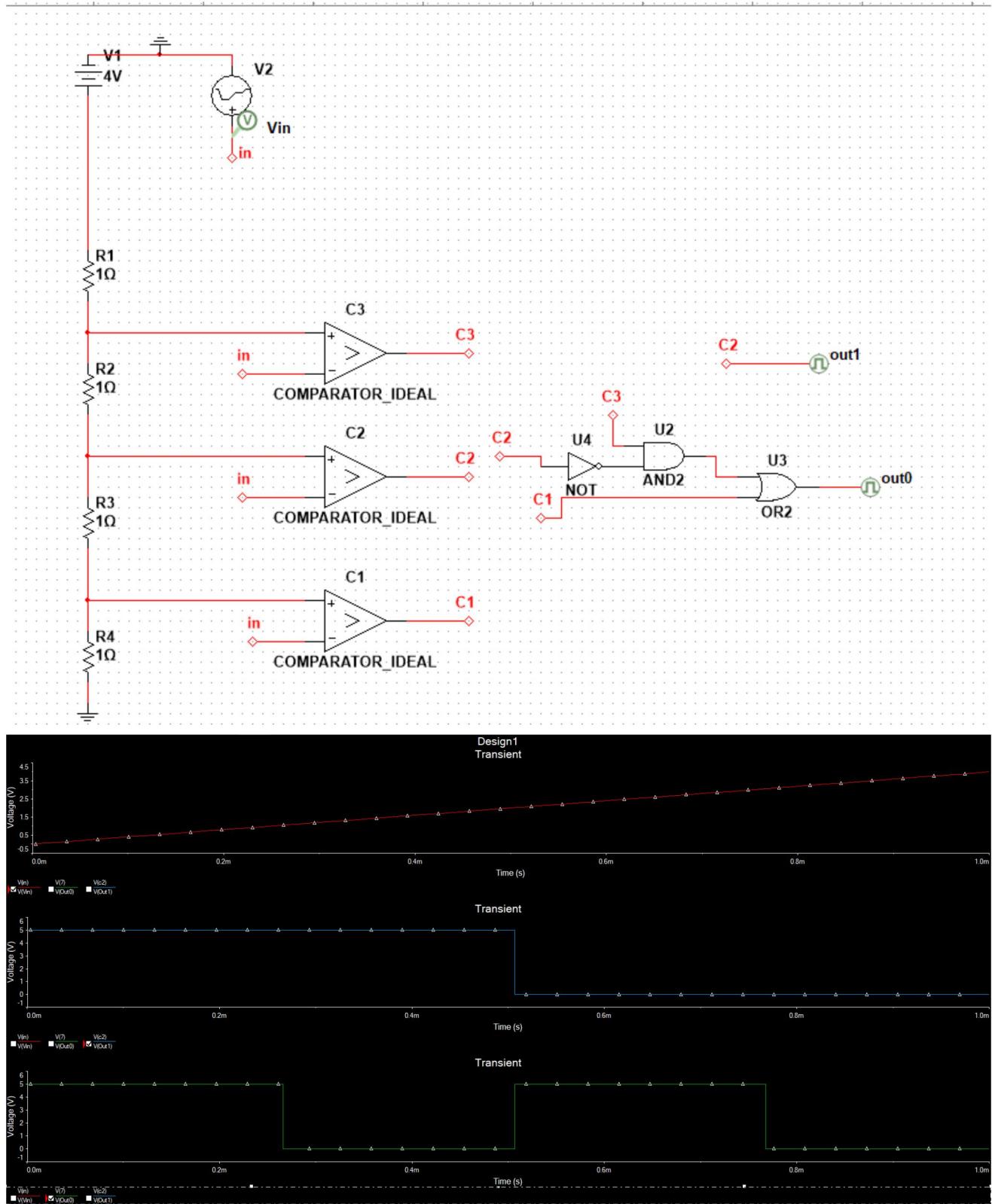Question assigned to the following page: [3](#)



Out1 is the first digit of the output, and out0 is the second digit of the output.

* Please submit the softcopy of your solutions to the problems on gradescope.

* All flow charts and codes should be enclosed in your solutions.

Question assigned to the following page: [3](#)

** Discussion on methodology is allowed, yet, the assignment should be done individually. Plagiarism, once found, grades zero for the whole homework assignment!*

